



University of  
**Nottingham**

UK | CHINA | MALAYSIA

# Single-Cycle CPU

Dr. Heng Yu

AY2022-23, Spring Semester  
**COMP1047: Systems and Architecture**  
Week 6

## Today's outline

- ✓ Introducing the MIPS CPU design
- ✓ Analyzing the instruction set
- ✓ Constructing the datapath
- ✓ Datapath with control unit




- ✓ CPU performance factors
  - Instruction count, determined by ISA and compiler
  - CPI and cycle time, determined by CPU hardware
- ✓ We will examine two MIPS implementations
  - A simplified version
  - A more realistic pipelined version
- ✓ Simple subset, shows most aspects
  - Memory reference: **lw, sw**
  - Arithmetic/logical: **add, sub, addi, and, or, slt**
  - Control transfer: **beq, j**



## Instruction execution process (general)

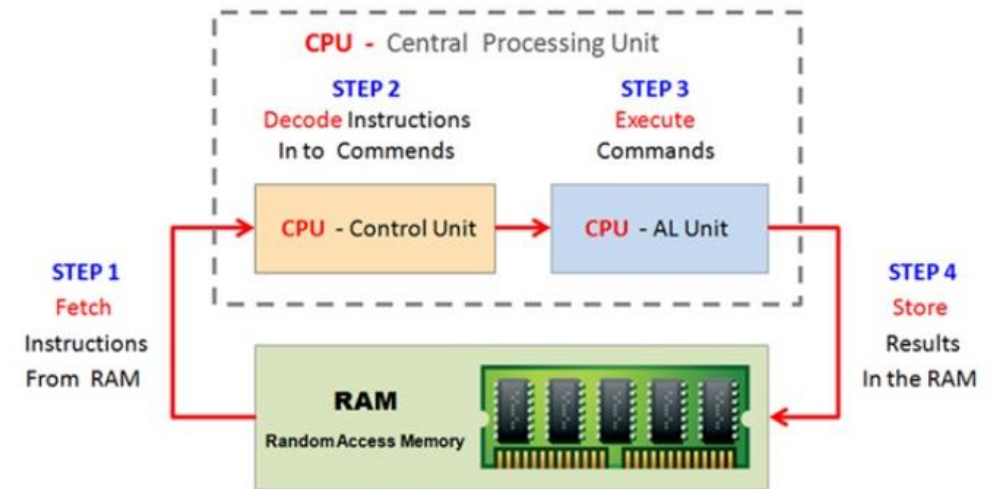1. PC -> instruction memory, fetch instruction
2. Register numbers -> register file, read registers
3. Depending on instruction types
  1. Use ALU to calculate
    1. Arithmetic result
    2. Memory address for load/store
    3. Branch target address
  2. Access data memory for load/store
4. PC -> target address or PC + 4



0xA000 0114

0xA000 0110

0xA000 010C

0xA000 0108

0xA000 0104

0xA000 0100

or \$10, \$2, \$7

beq \$6, \$7, L1

lw \$10, 2(\$7)


add \$6, \$7, \$8

sub \$1, \$2, \$0

add \$1, \$2, \$0

## Instruction execution process (general)

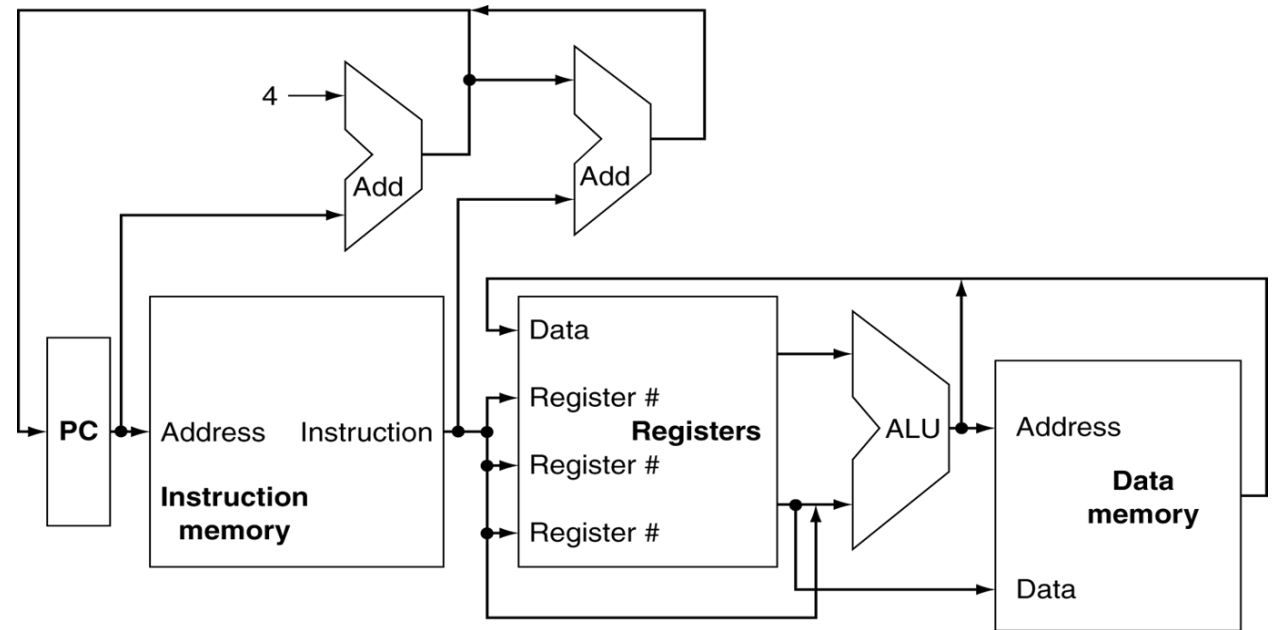
1. PC -> instruction memory, fetch instruction
2. Register numbers -> register file, read registers
3. Depending on instruction types
  1. Use ALU to calculate
    1. Arithmetic result
    2. Memory address for load/store
    3. Branch target address
  2. Access data memory for load/store
4. PC -> target address or PC + 4





## Instruction execution process (general)

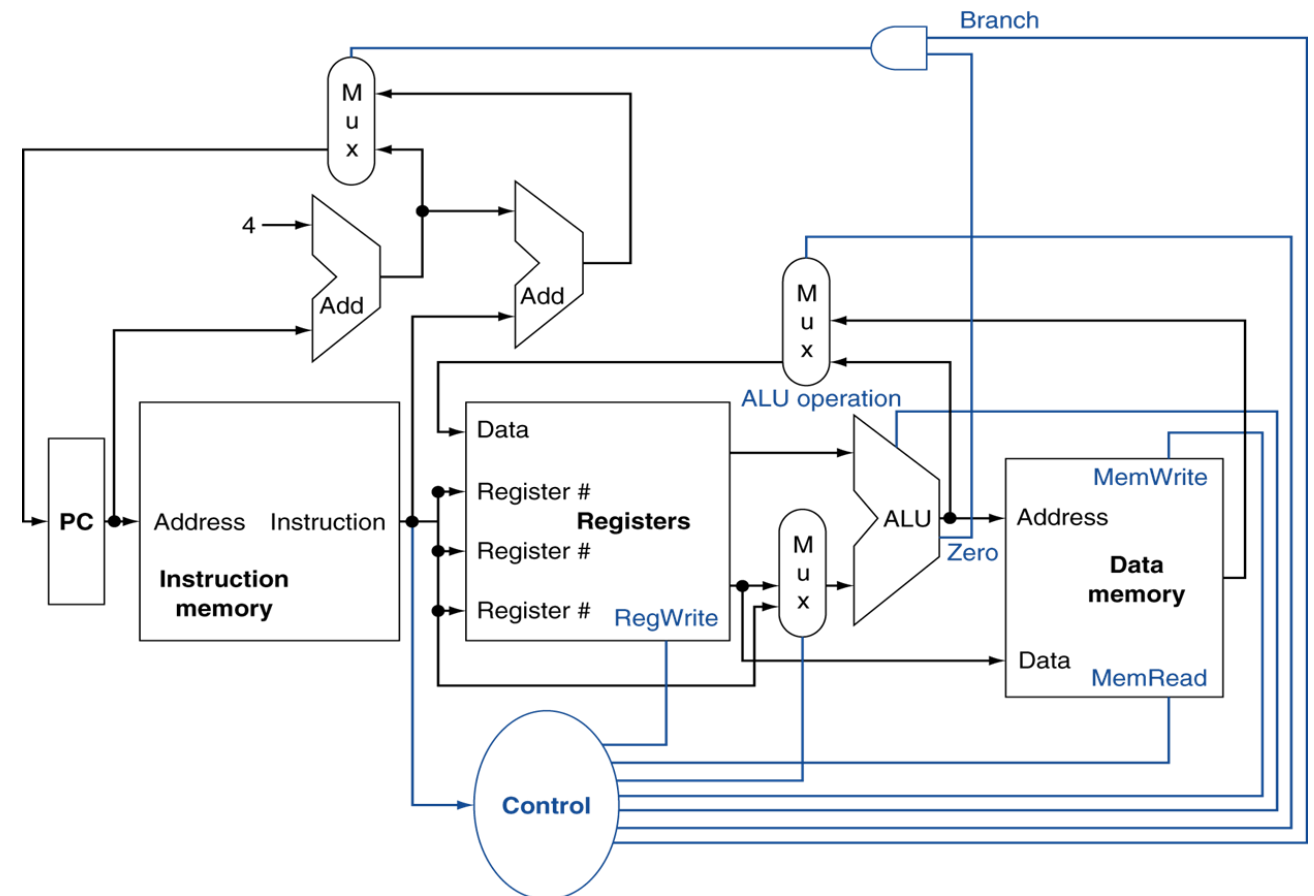1. PC -> instruction memory, fetch instruction
2. Register numbers -> register file, read registers
3. Depending on instruction types
  1. Use ALU to calculate
    1. Arithmetic result
    2. Memory address for load/store
    3. Branch target address
  2. Access data memory for load/store
4. PC -> target address or PC + 4




## Logic Design Basics

- ✓ Information encoded in binary
  - Low voltage = 0, High voltage = 1
  - One wire per bit
  - Multi-bit data encoded on multi-wire buses
- ✓ Combinational element
  - Operate on data
  - Output is a function of input
- ✓ State (sequential) elements
  - Store information


### ◆ AND-gate

◆  $Y = A \& B$

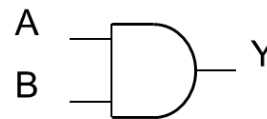


### ◆ Multiplexer

◆  $Y = S ? I1 : I0$

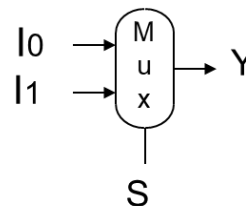


### ◆ Adder

◆  $Y = A + B$

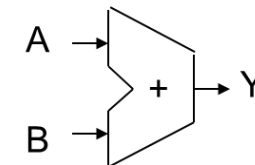





### ◆ Arithmetic/Logic Unit

◆  $Y = F(A, B)$

 
    
## Sequential Elements


- Register: stores data in a circuit
  - Uses a clock signal to determine when to update the stored value
  - Rising-Edge-triggered**: update when Clk changes from 0 to 1
- Register with **write control**
  - Only updates on clock edge **when write control input is 1**
  - Used when stored value is required later





## How to design a Processor?

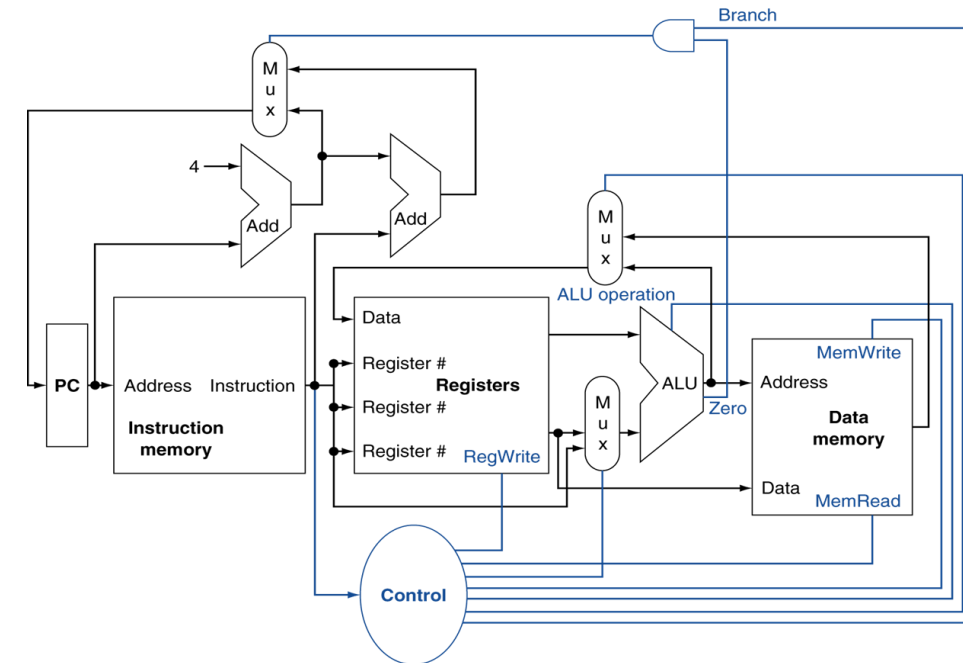1. Analyze the instruction set (datapath requirements) (D)
  - The meaning of each instruction is given by the *register transfers*
  - Datapath must include storage element
  - Datapath must support each register transfer
2. Select the set of datapath components and establish clocking methodology (D)
3. Assemble datapath meeting the requirements (D)
4. Analyze the implementation of each instruction to determine the setting of control points that affect the register transfer (C)
5. Assemble the control logic (C)



add \$t3, \$t1, \$t2

## Today's outline

- ✓ Introducing the MIPS CPU design
- ✓ Analyzing the instruction set
- ✓ Constructing the datapath
- ✓ Datapath with control unit



# Analyzing the Instruction Set

## Our example: A MIPS Subset

### ✓ R-Type:

- ★ `add rd, rs, rt`
- ★ `sub rd, rs, rt`
- ★ `and rd, rs, rt`
- ★ `or rd, rs, rt`
- ★ `slt rd, rs, rt`

### ✓ Load/Store:



- ★ `lw rt,rs,imm16`
- ★ `sw rt,rs,imm16`

### ✓ Imm operand:

- ★ `addi rt,rs,imm16`

### ✓ Branch:

- ★ `beq rs,rt,imm16`

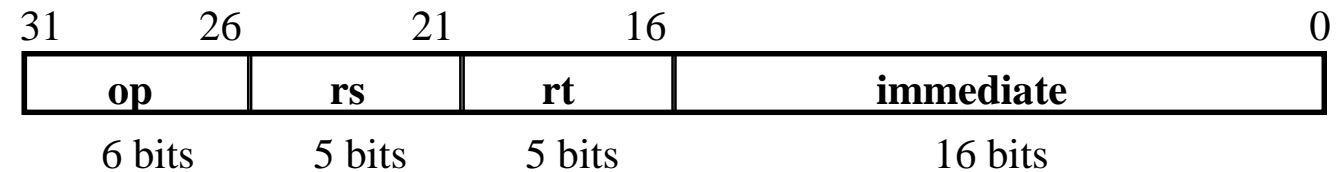 



# Analyzing the Instruction Set

RTL (Register Transfer Language) gives the semantics of the instructions

$MEM[PC] = op \mid rs \mid rt \mid rd \mid shamt \mid funct$   
or  $= op \mid rs \mid rt \mid Imm16$

Inst.	Register transfers
ADD	$R[rd] \leftarrow R[rs] + R[rt]; \quad PC \leftarrow PC + 4$
SUB	$R[rd] \leftarrow R[rs] - R[rt]; \quad PC \leftarrow PC + 4$
LOAD	$R[rt] \leftarrow MEM[R[rs] + sign\_ext(Imm16)]; \quad PC \leftarrow PC + 4$
STORE	$MEM[R[rs] + sign\_ext(Imm16)] \leftarrow R[rt]; \quad PC \leftarrow PC + 4$
ADDI	$R[rt] \leftarrow R[rs] + sign\_ext(Imm16); \quad PC \leftarrow PC + 4$
BEQ	if ( $R[rs] == R[rt]$ ) then $PC \leftarrow PC + 4 + sign\_ext(Imm16) \mid \mid 00$ else $PC \leftarrow PC + 4$

0xA000 0114

0xA000 0110

0xA000 010C

0xA000 0108

0xA000 0104

0xA000 0100

or \$10, \$2, \$7

beq \$6, \$7, L1

lw \$10, 2(\$7)

add \$6, \$7, \$8

sub \$1, \$2, \$0







add \$1, \$2, \$0

# Analyzing the Instruction Set
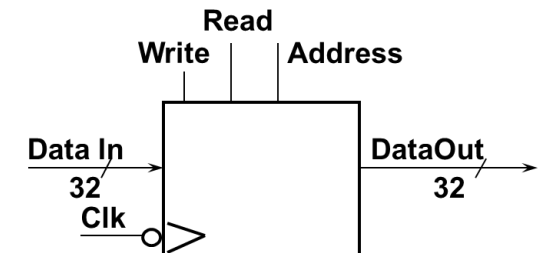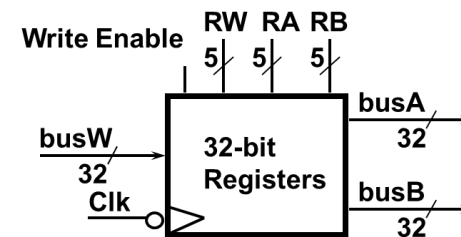 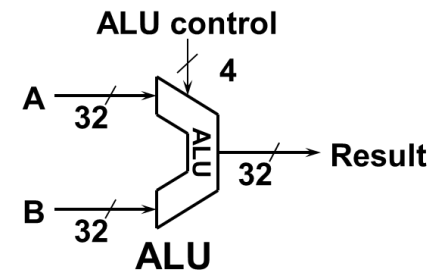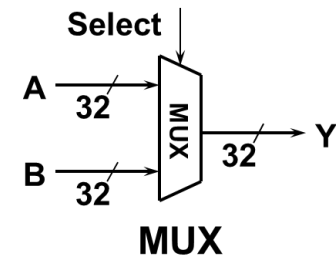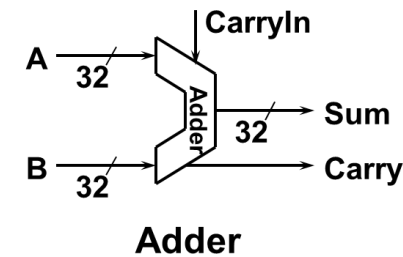
## What hardware are needed?

After checking the register transfers, we can conclude that datapath needs the following hardware:

- ➔ Memory
  - store instructions and data
- ➔ Registers (32 x 32)
  - read RS
  - read RT
  - Write RT or RD
- ➔ PC
- ➔ Extender for zero- or sign-extension
- ➔ Calculating values in registers or extended immediate (ALU)
- ➔ Add 4 or extended immediate to PC






## Today's outline

- ✓ Introducing the MIPS CPU design
- ✓ Analyzing the instruction set
- ✓ Constructing the datapath
- ✓ Datapath with control unit

## Sequential components for datapath:
 
### Register:


- ✓ Similar to the D Flip Flop except
  - 32-bit input and output
  - Write Enable input
- ✓ Write Enable:
  - Negated (0): **Data Out** will not change
  - Asserted (1): **Data Out** will become **Data In**



## Sequential components for datapath:
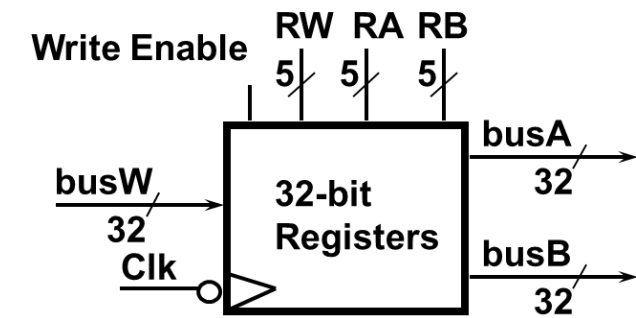
### Register file:


- ✓ Consists of 32 registers:
  - Two 32-bit output busses: **busA** and **busB**
  - One 32-bit input bus: **busW**
- ✓ Register is selected by:
  - **RA** selects the register to put on **busA** (data)
  - **RB** selects the register to put on **busB** (data)
  - **RW** selects the register to be written via **busW** (data) when **Write Enable** is 1
- ✓ Clock input (CLK)
  - The **CLK** input is a factor ONLY during write operation
  - During read, behaves as a combinational circuit



## Sequential components for datapath:
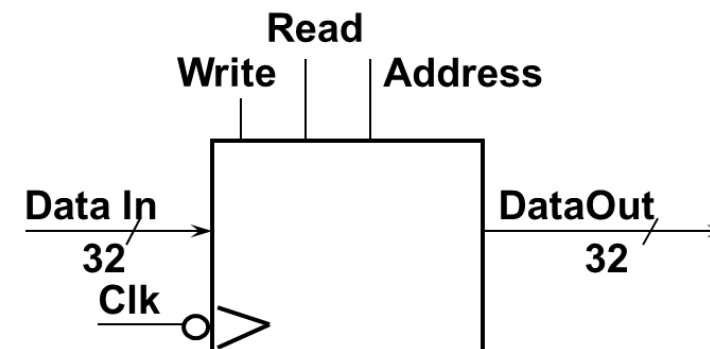
### Memory:

- ✓ One input bus: **Data In**
- ✓ One output bus: **Data Out**
- ✓ Word is selected by:
  - **Address** selects the word to put on **Data Out**
  - **Write Enable** = 1: address selects the memory word to be written via the **Data In** bus
- ✓ Clock input (CLK)
  - The **CLK** input is a factor during write and read operations



0xA000 0114

0xA000 0110

0xA000 010C

0xA000 0108

0xA000 0104

0xA000 0100

or \$10, \$2, \$7

beq \$6, \$7, L1

lw \$10, 2(\$7)

add \$6, \$7, \$8

sub \$1, \$2, \$0


add \$1, \$2, \$0

## Assembling the datapath

**Instruction fetching** is divided into two major steps:

- ✓ Fetch the instruction: **mem[ PC ]**
- ✓ Update the program counter:
  - Sequential code:  $PC \leftarrow PC + 4$
  - Branch and Jump:  $PC \leftarrow \text{"Something else"}$

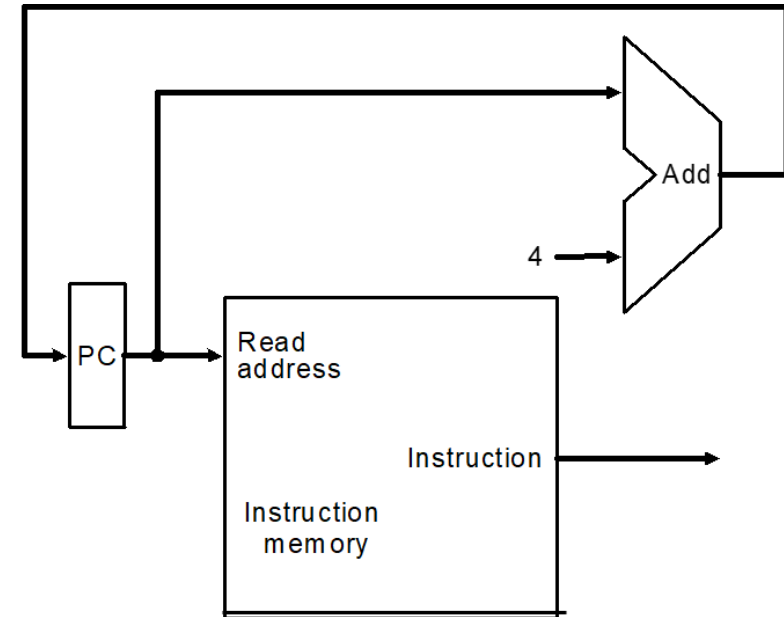$MEM[ PC ] = op \mid rs \mid rt \mid rd \mid shamt \mid funct$   
 $or = op \mid rs \mid rt \mid Imm16$



0xA000 0114

0xA000 0110

0xA000 010C

0xA000 0108

0xA000 0104

0xA000 0100

or \$10, \$2, \$7

beq \$6, \$7, L1

lw \$10, 2(\$7)

add \$6, \$7, \$8



sub \$1, \$2, \$0

add \$1, \$2, \$0



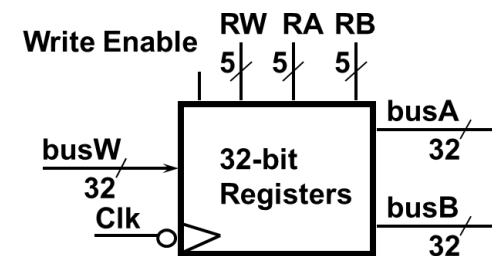 
## Assembling the datapath

- ✓ **Arithmetic/logical operations:**  $R[rd] \leftarrow R[rs] \text{ op } R[rt]$
- ✓ E.g., R-type instructions: add, sub, and, or, etc.
- ✓ **RA, RB, RW** come from instruction's **rs, rt, rd** fields
- ✓ ALU and RegWrite: control logic after decoding




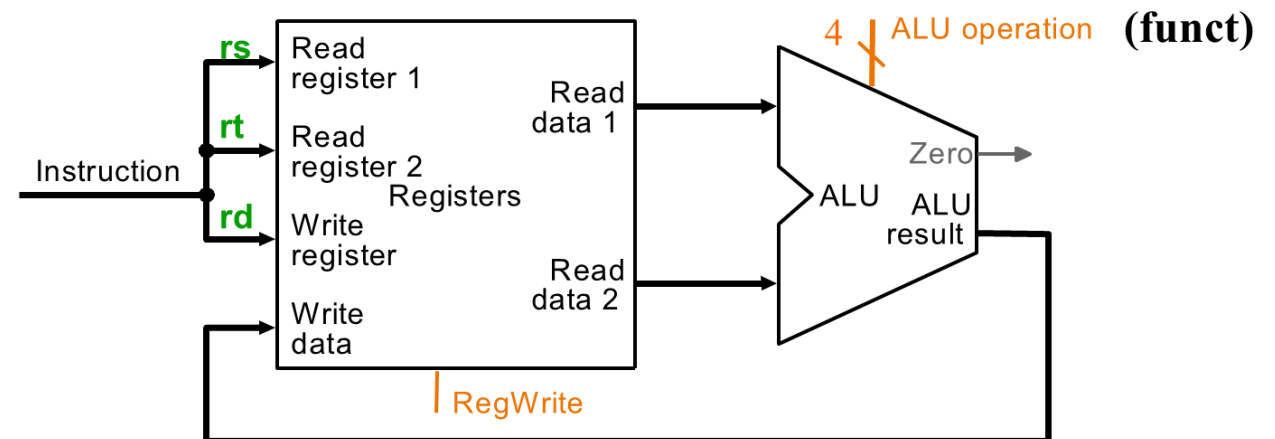
**ADD**      $R[rd] \leftarrow R[rs] + R[rt];$       $PC \leftarrow PC + 4$   
**SUB**      $R[rd] \leftarrow R[rs] - R[rt];$       $PC \leftarrow PC + 4$


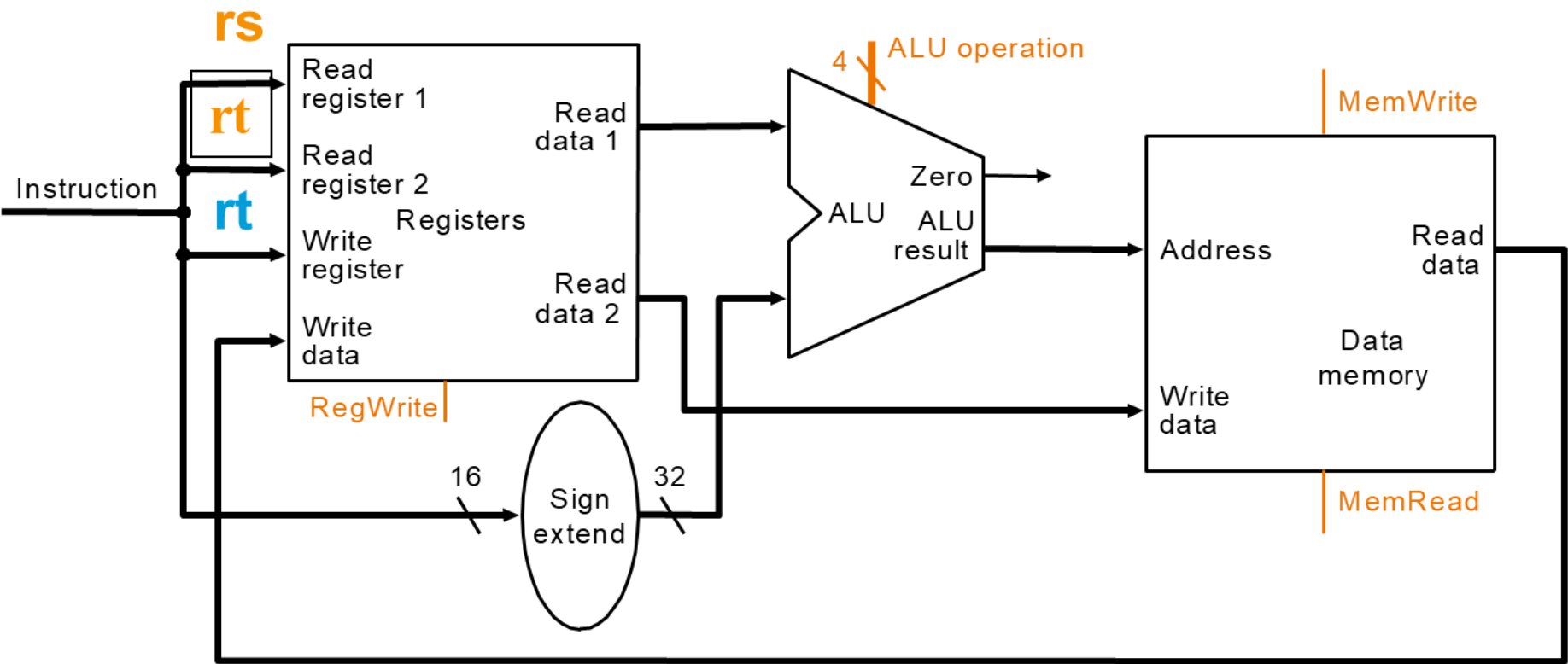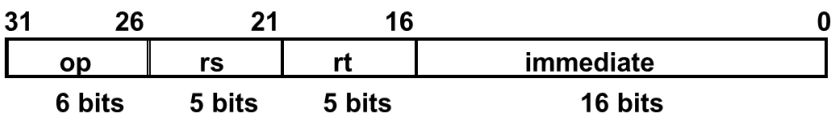
## Assembling the datapath

load operations: lw rt, imm16(rs)

$R[rt] \leftarrow MEM[R[rs] + sign\_ext(Imm16)];$



lw \$10, 4(\$9)



0xA000 0108  
0xA000 0104  
0xA000 0100

xxxx ... xxxx
0100 ... 1001
0000 ... 0100

## Assembling the datapath

- store operations: `sw`, `st`, `imm16(rs)`

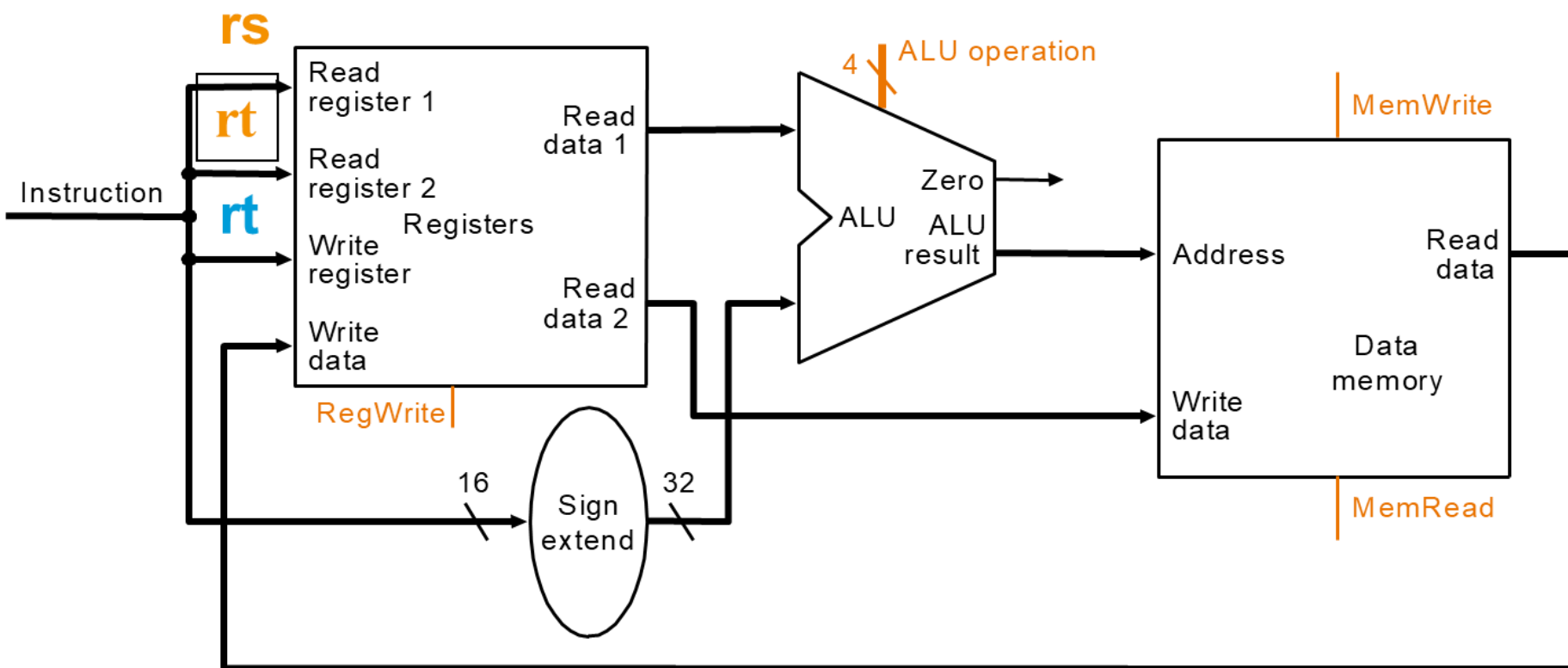 **MEM[ R[rs] + sign\_ext(Imm16) ] ← R[rt];**



SW \$10, 4 (\$9)

0xA000 0108

XXXX ... XXXX

0xA000 0104


0100 ... 1001

0xA000 0100

0000 ... 0100

## Assembling the datapath

### ✓ R-Type/Load/Store Datapath

 

## Assembling the datapath

✓ **Branch operations:** `beq rs, rt, imm16`

`mem[PC]`

`Equal ← R[rs] == R[rt]`

`if (Equal)`

`PC ← PC + 4 + ( SignExt(imm16) x 4 )`


`else`

`PC ← PC + 4`

Fetch inst. from memory

Calculate branch condition

Calculate next inst. Address

 



## Assembling the datapath

✓ **Branch operations:** `beq rs, rt, imm16`

`mem[PC]`


`Equal ← R[rs] == R[rt]`

`if (Equal)`

`PC ← PC + 4 + ( SignExt(imm16) x 4 )`


`else`

`PC ← PC + 4`

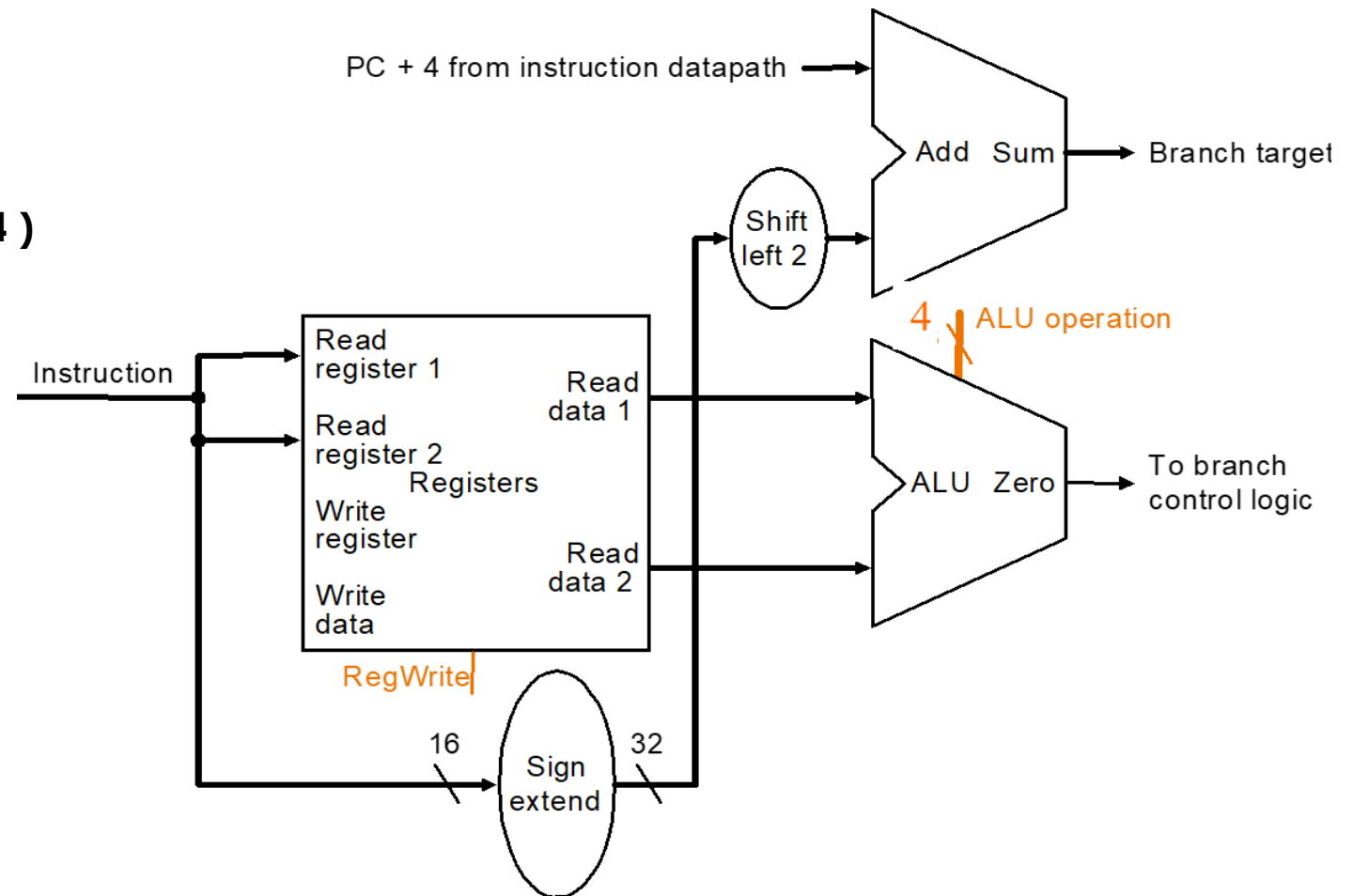




## A Single-Cycle Datapath

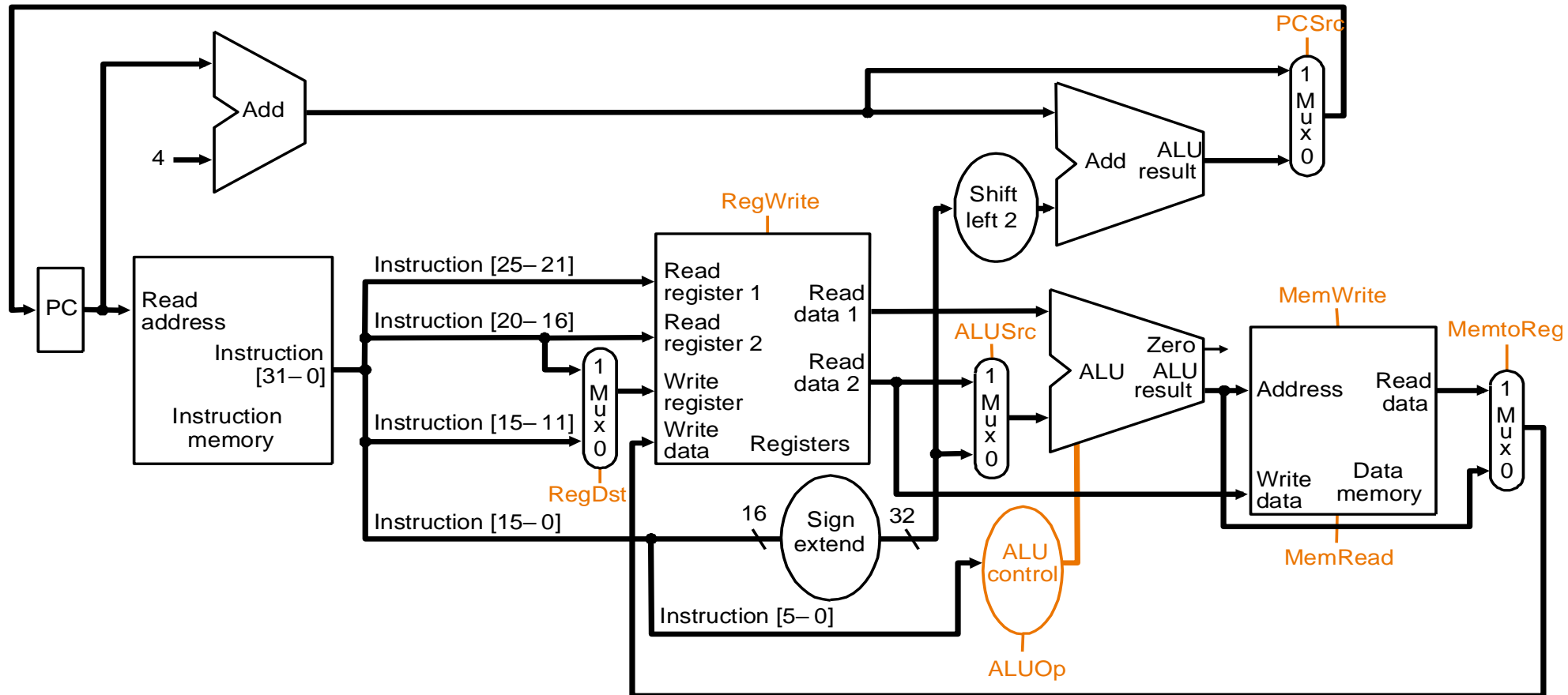



# Building the Datapath


## Dataflow during **add**

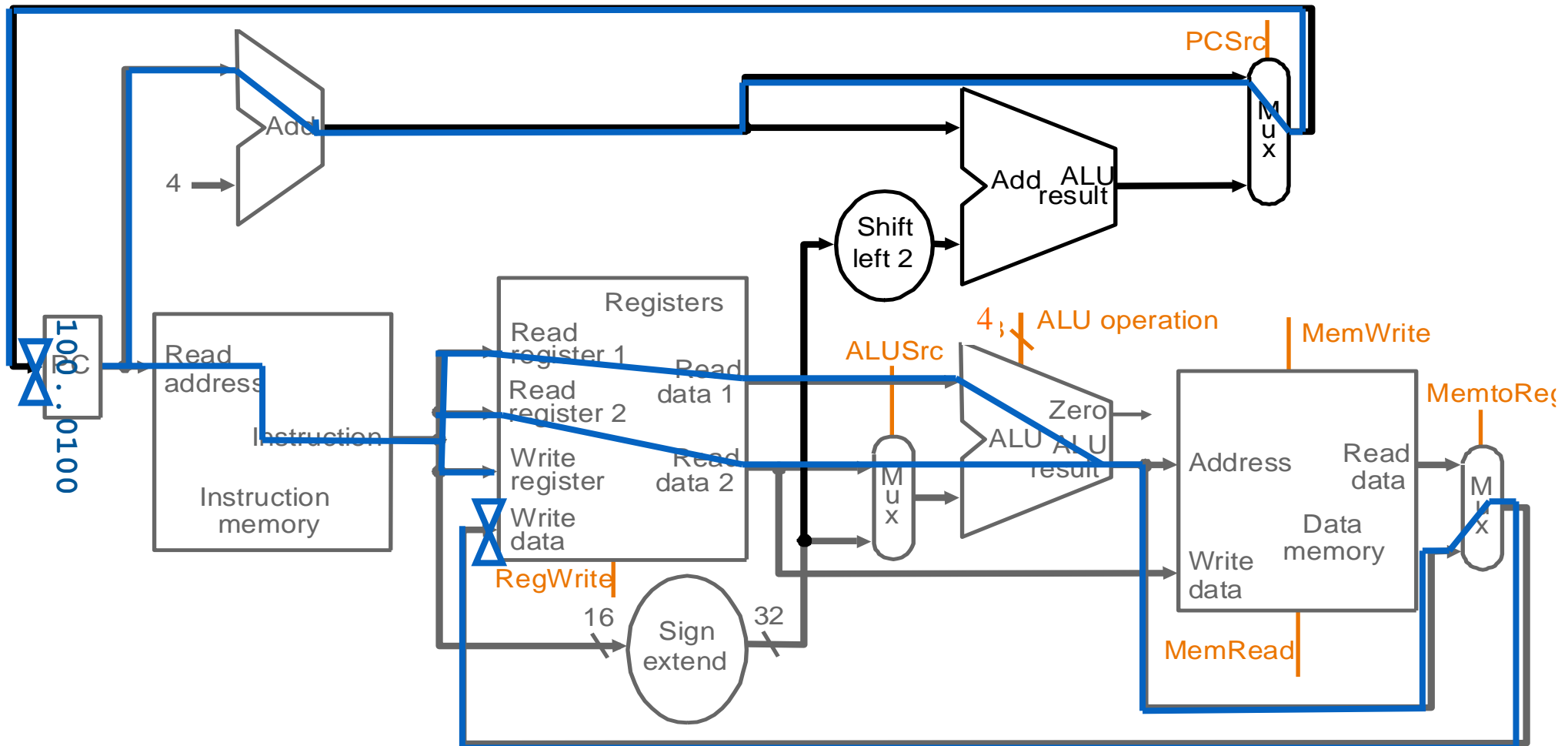

## Today's outline

- ✓ Introducing the MIPS CPU design
- ✓ Analyzing the instruction set
- ✓ Constructing the datapath
- ✓ Datapath with control unit

## Datapath with control unit

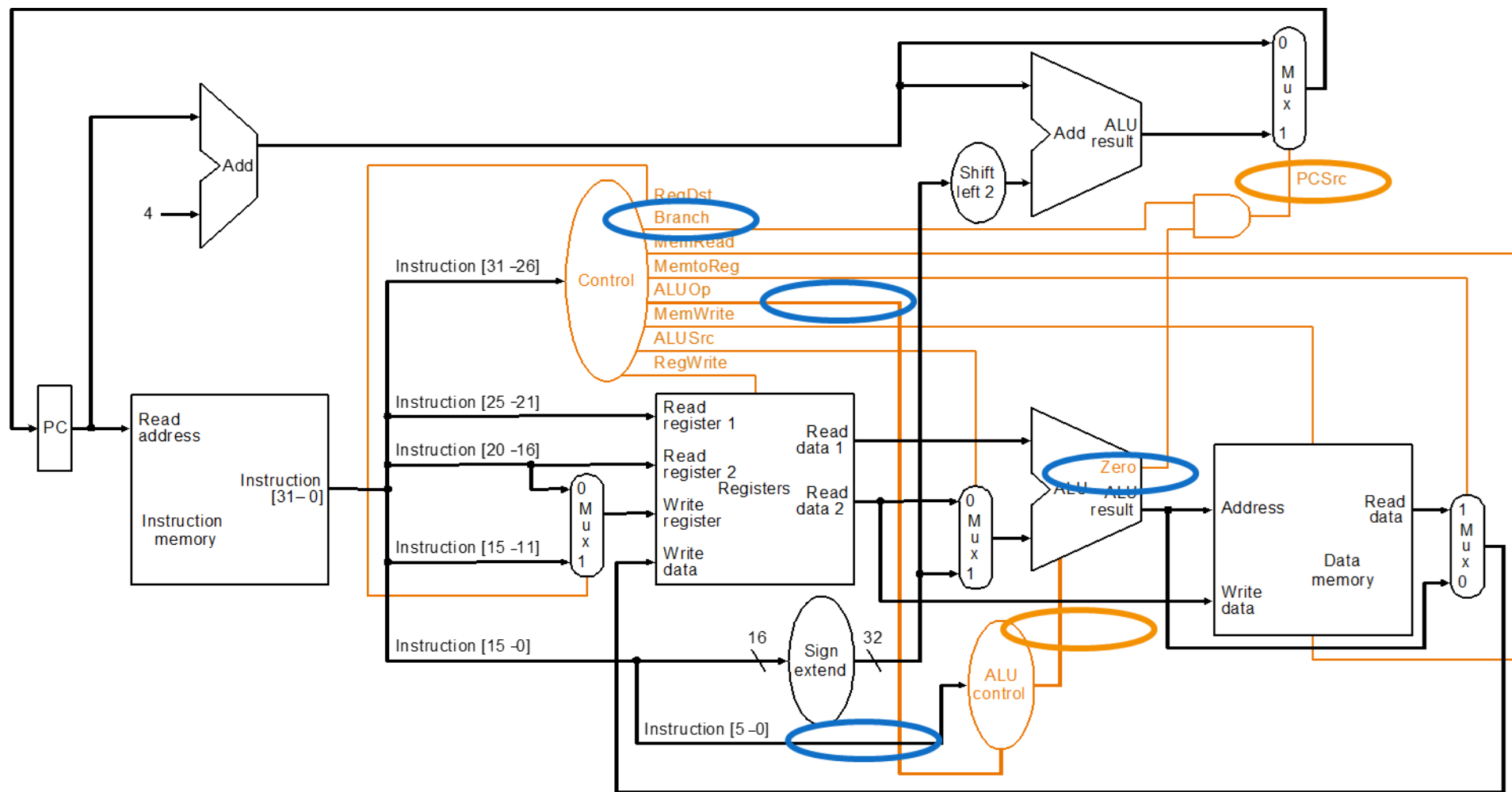






## Truth Table of Control Signals (6 Inputs and 9 Outputs)


See Appendix A

	func	op	10 0000	10 0010	We Don't Care :-)		
			00 0000	00 0000	10 0011	10 1011	00 0100
			add	sub	lw	sw	beq
RegDst			1	1	0	x	x
ALUSrc			0	0	1	1	0
MemtoReg			0	0	1	x	x
RegWrite			1	1	1	0	0
MemRead			0	0	1	0	0
MemWrite			0	0	0	1	0
Branch			0	0	0	0	1
ALUop1			1	1	0	0	0
ALUop0			0	0	0	0	1

 
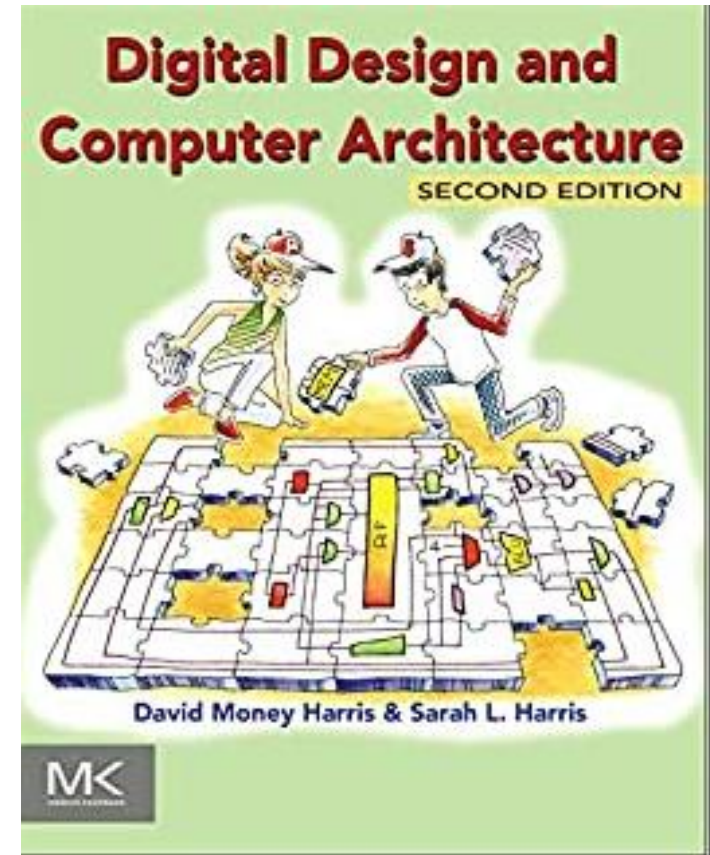
# Summary

- Single cycle datapath =>  $CPI=1$ , clock cycle time long
- MIPS makes control easier
  - Instructions in the same size
  - Source registers always in the same place
  - Immediates in the same size and location
  - Operations always on registers or immediates
- Not covered in this lecture
  - Designing the control unit
  - J-type instruction
  - Read the corresponding chapters in textbooks.





University of  
**Nottingham**

UK | CHINA | MALAYSIA

**Thank you.**